
#### Segment A

BR	BIN	0/1
0	0000	1
1	0001	0
2	0010	1
3	0011	1
4	0100	0
5	0101	1
6	0110	1
7	0111	1
8	1000	1
9	1001	1
Α	1010	1
В	1011	0
С	1100	1
D	1101	0
E	1110	1
F	1111	1

B1E	30	00	01	11	10
	00	1		1	1
B3B2	01		1	1	1
	11	1		1	1
	10	1	1		1

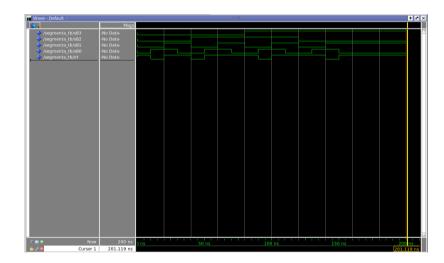


$$F = B_1B_0 + B_3B_1 + B_3B_2B_0 + B_2B_1 + B_3B_1B_0 + B_3B_2B_1 + B_2B_1B_0$$

#### Segment B

BR	BIN	0/1
0	0000	1
1	0001	1
2	0010	1
3	0011	1
4	0100	1
5	0101	0
6	0110	0
7	0111	1
8	1000	1
9	1001	1
Α	1010	1
В	1011	0
С	1100	0
D	1101	1
E	1110	0
F	1111	0

B1B(	0	00	01	11	10
	00	1	1	1	1
B3B2	01	1		1	
	11		1		
	10	1	1		1

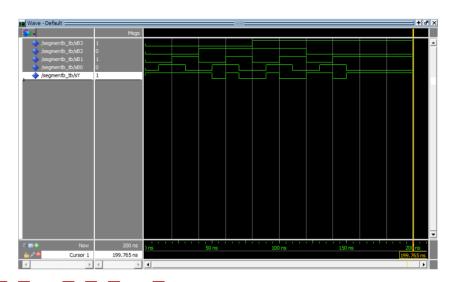


 $F = B_3B_2 + B_3B_1B_0 + B_3B_2B_0 + B_3B_1B_0 + B_3B_1B_0$ 

## Segment C

BR	BIN	0/1
0	0000	1
1	0001	1
2	0010	0
3	0011	1
4	0100	1
5	0101	1
6	0110	1
7	0111	1
8	1000	1
9	1001	1
Α	1010	1
В	1011	1
С	1100	0
D	1101	1
Е	1110	0
F	1111	0

B1E	30	00	01	11	10
	00	1	1	1	
B3B2	01	1	1	1	1
	11		1		
	10	1	1	1	1

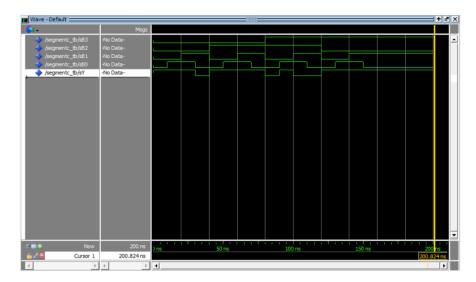

$$F = B_3B_1 + B_3B_2 + B_3B_2 + B_2B_1B_0 + B_3B_0$$

## Segment D

BR	BIN	0/1
0	0000	1
1	0001	0
2	0010	1
3	0011	1
4	0100	0
5	0101	1
6	0110	1
7	0111	0
8	1000	1
9	1001	1
Α	1010	0
В	1011	1
С	1100	1
D	1101	1
E	1110	1
F	1111	0

B1B	0	00	01	11	10
	00	1		1	1
B3B2	01		1		1
	11	1	1		1
	10	1	1	1	




 $F = B_3B_1 + B_2B_1B_0 + B_3B_2B_0 + B_2B_1B_0 + B_2B_1B_0$ 

## Segment E

BR	BIN	0/1
0	0000	1
1	0001	0
2	0010	1
3	0011	0
4	0100	0
5	0101	0
6	0110	1
7	0111	0
8	1000	1
9	1001	0
Α	1010	1
В	1011	1
С	1100	1
D	1101	1
E	1110	1
F	1111	1

B16	30	00	01	11	10
	00	1			1
B3B2	01				1
	11	1	1	1	1
	10	1		1	1

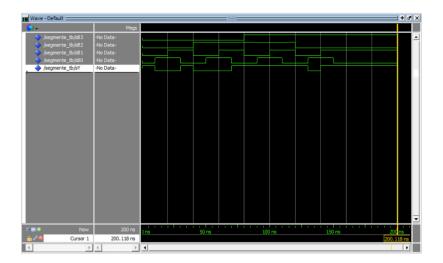


$$F = B_1 B_0 + B_3 B_1 + B_3 B_2 + B_2 B_1 B_0$$

# <u>Segment F</u>

BR	BIN	0/1
0	0000	1
1	0001	0
2	0010	0
3	0011	0
4	0100	1
5	0101	1
6	0110	1
7	0111	0
8	1000	1
9	1001	1
Α	1010	1
В	1011	1
С	1100	1
D	1101	0
E	1110	1
F	1111	1

B1B	0	00	01	11	10
	00	1			
B3B2	01	1	1		1
	11	1		1	1
	10	1	1	1	1

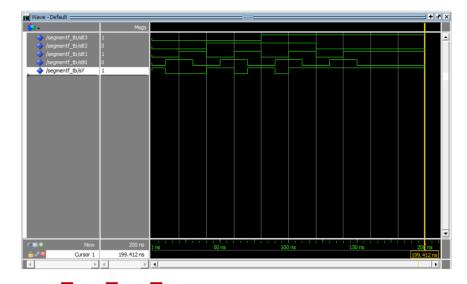


 $F = B_3B_1 + B_3B_2 + B_1B_0 + B_2B_1B_0 + B_3B_2B_1$ 

# Segment G

BR	BIN	0/1
0	0000	0
1	0001	0
2	0010	1
3	0011	1
4	0100	1
5	0101	1
6	0110	1
7	0111	0
8	1000	1
9	1001	1
Α	1010	1
В	1011	1
С	1100	0
D	1101	1
E	1110	1
F	1111	1

B16	30	00	01	11	10
	00			1	1
B3B2	01	1	1		1
	11		1	1	1
	10	1	1	1	1

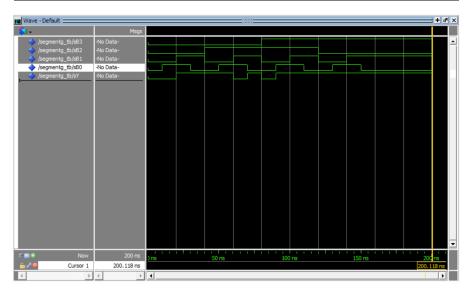

$$F = B_1B_0 + B_3B_0 + B_3B_2B_1 + B_3B_2B_1 + B_2B_1$$